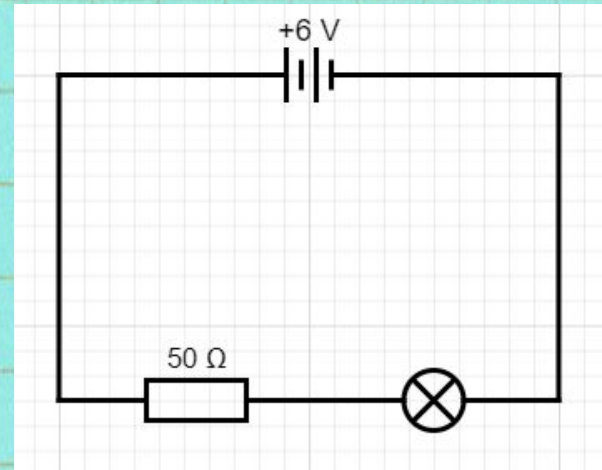


## Challenge #11



### Suggested circuit


Battery, resistor and bulb



### How circuit works

The resistor reduces the flow of current through the bulb

### Circuit setup using components

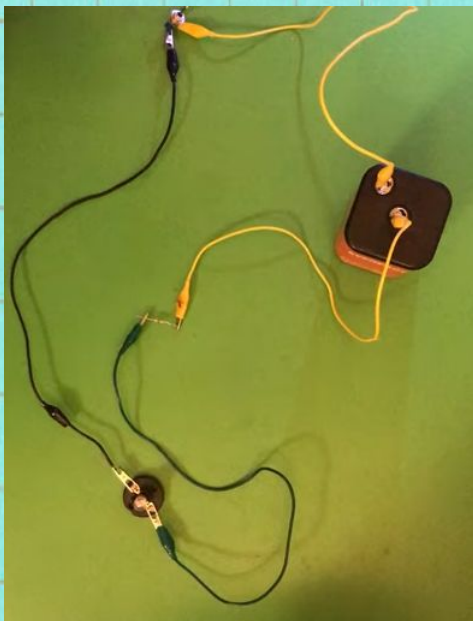

### Link to video of circuit in action

<https://youtu.be/da7hbxg91gw>

