
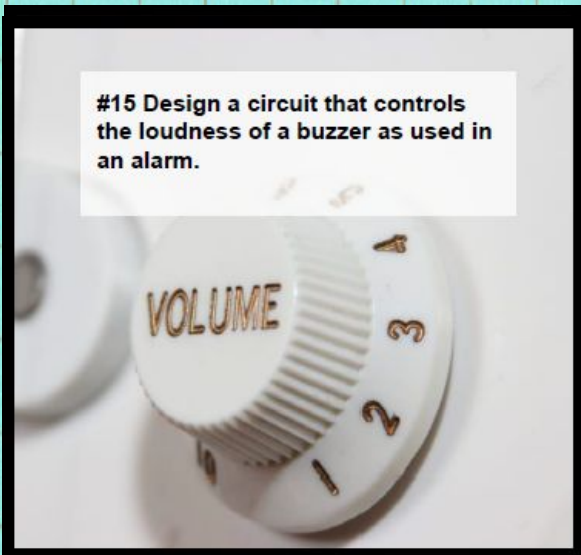


Challenge #15

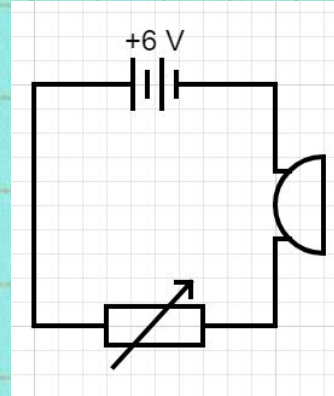

Suggested circuit


Battery, variable resistor and buzzer.



How circuit works.

As the resistance of the variable resistor is decreased, the current through the buzzer increases and it becomes louder.

Circuit setup using components

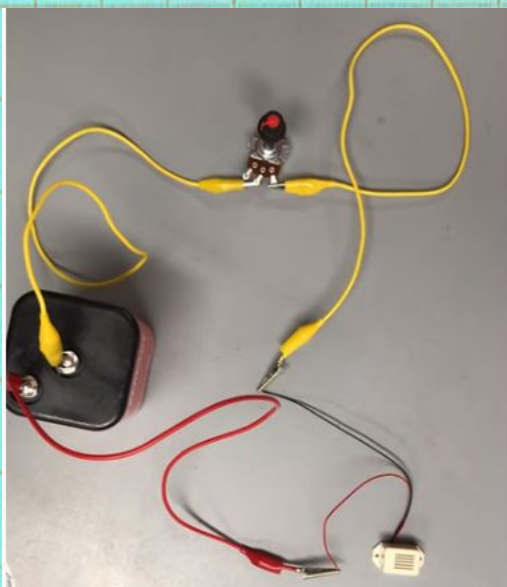

Link to video of circuit in action

https://youtu.be/S_qDZ7LUxRc

