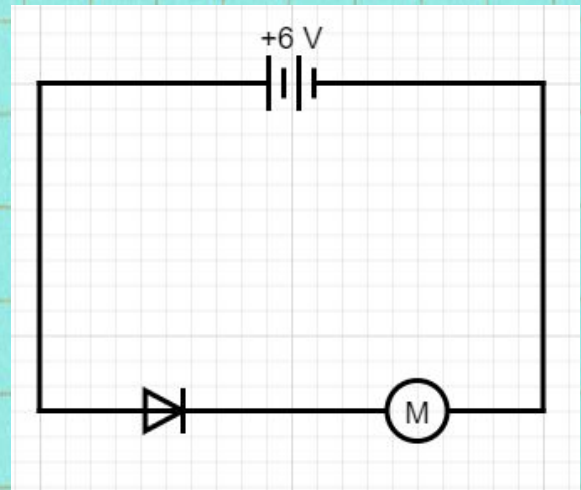


Challenge #16



Suggested circuit


Battery, diode and motor



How circuit works

Diodes only allow current to flow in one direction.

Circuit setup using components

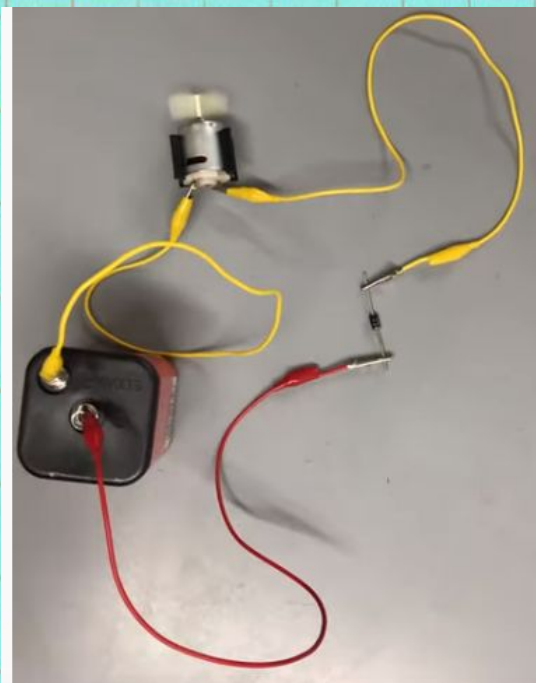

Link to video of circuit in action

<https://youtu.be/9Fwd9vNCLPY>

