
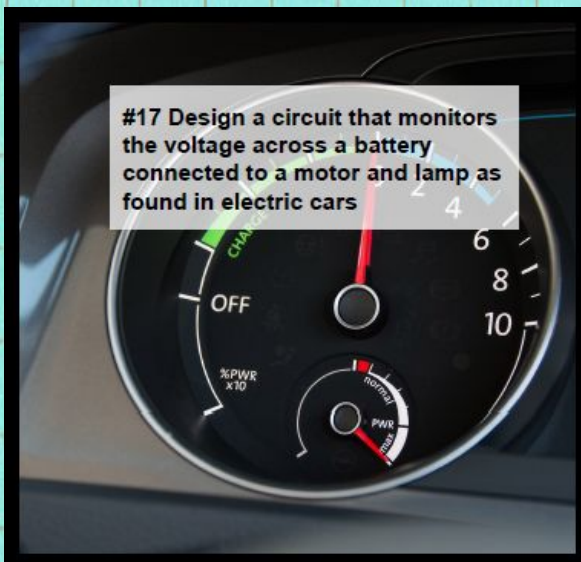


Challenge #17

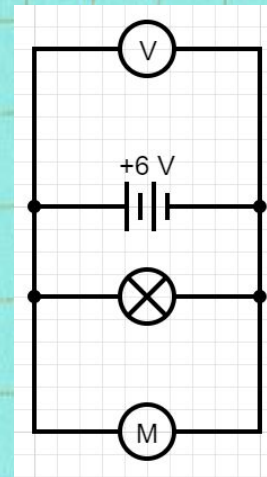

Suggested circuit


Battery, bulb, motor and voltmeter.



How circuit works

The voltmeter is connected in parallel to the battery. The motor and lamp are connected in parallel to the battery also.

Circuit setup using components

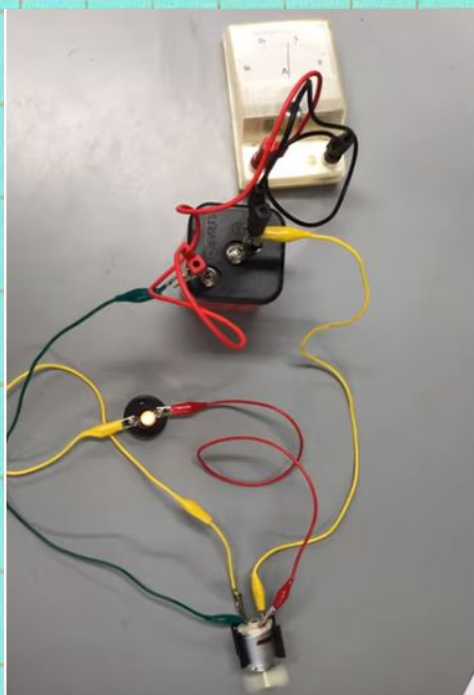

Link to video of circuit in action

<https://youtu.be/Rv8Wlwl2o3w>

