
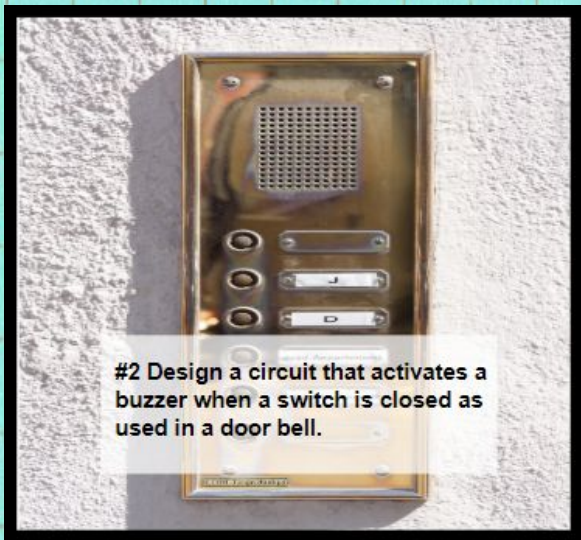


Challenge #2

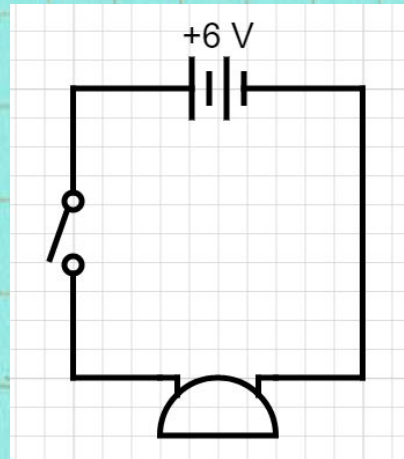

Suggested circuit


Battery, switch and buzzer



How circuit works

Closing the switch allows current to flow around the circuit causing the buzzer to make a sound

Circuit setup using components

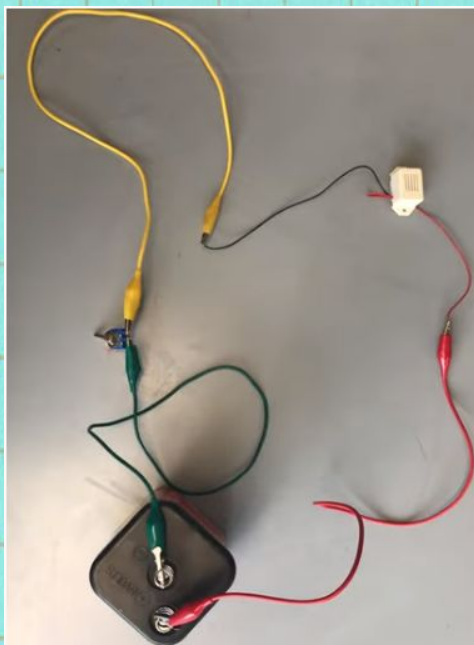

Link to video of circuit in action

https://youtu.be/iHa_Gj70CHI

