
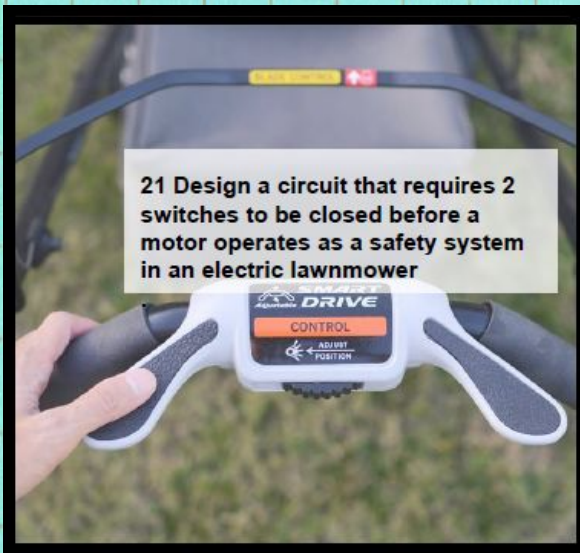


Challenge #21

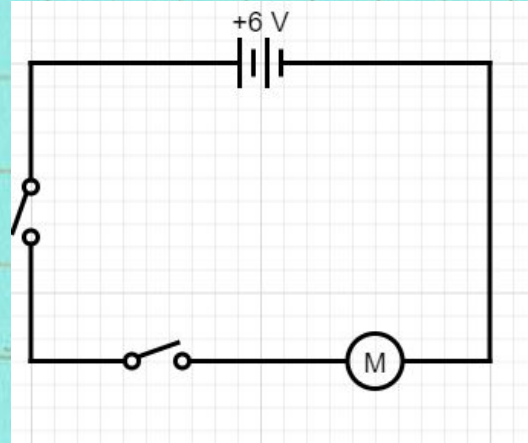

Suggested circuit

Battery, 2 switches and motor



How circuit works

Both switches are connected in series with a motor. Both switches must be closed for current to pass through the motor

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/suEDYMvGma8>

