
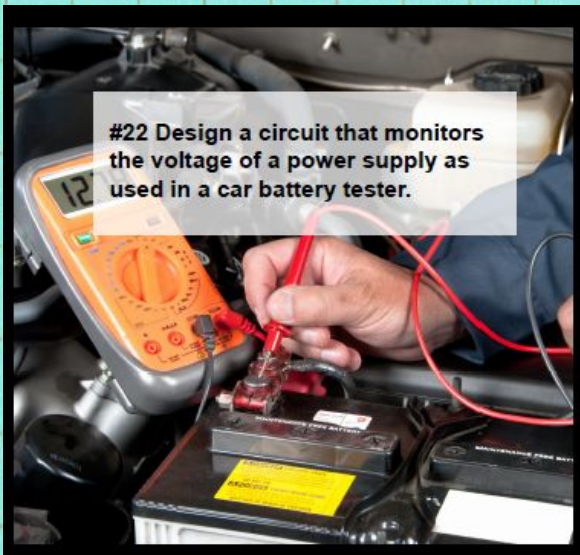


## Challenge #22

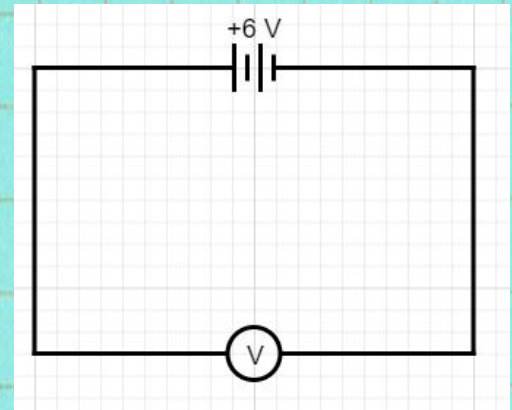

**Suggested circuit**  
Battery, voltmeter



### How circuit works

Voltmeters are always connected in parallel to devices.

**Circuit setup using components**

**Link to video of circuit in action**

<https://youtu.be/yEMRJCmMisl>

