
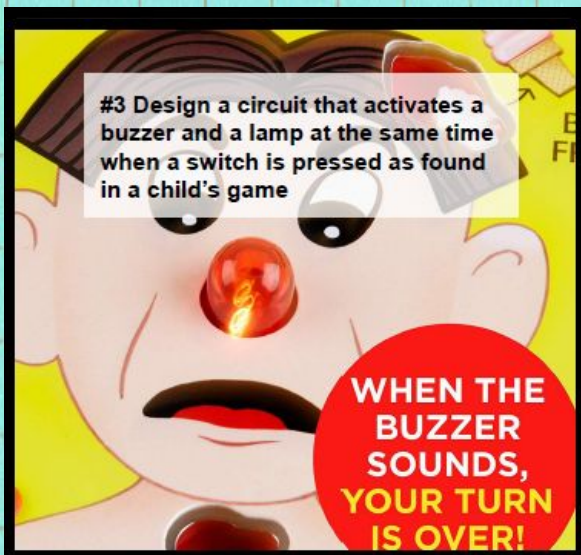


Challenge #3

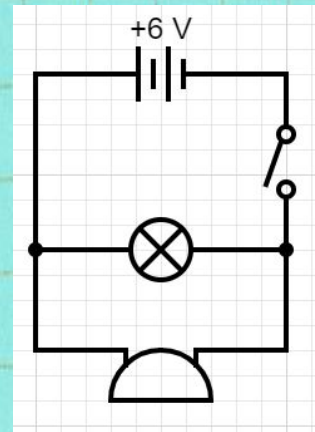

Suggested circuit

Battery, switch, buzzer and bulb



How circuit works

The bulb and buzzer are wired in parallel. Closing the switch allows current to flow around the circuit causing the buzzer to make a sound and the bulb to light.

Circuit setup using components



Link to video of circuit in action

<https://youtu.be/WyHF6dObxao>

