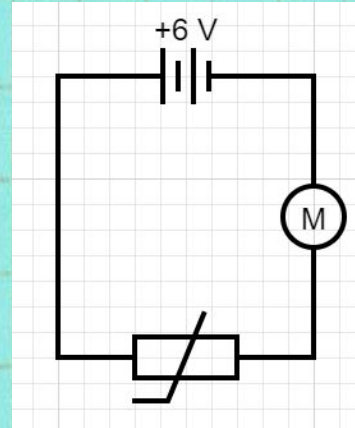


Challenge #4



Suggested circuit

Battery, motor and thermistor



How circuit works

As the temperature increases the resistance of the thermistor decreases. At high temperature the resistance is low enough to allow a large current to flow and activate the motor.

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/yIIIT8K5h7CE>

