
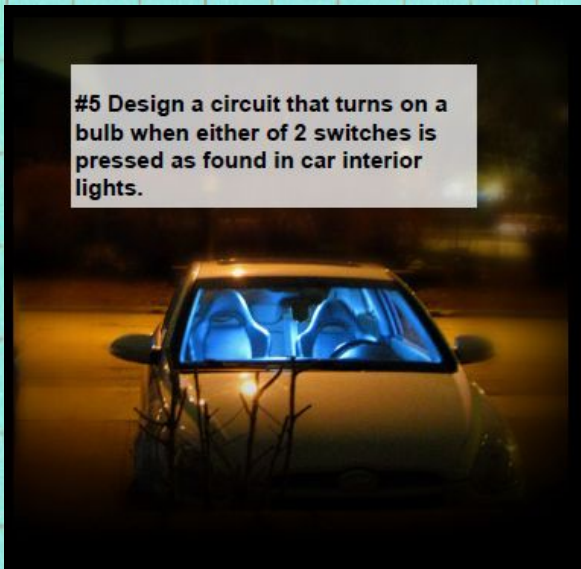


Challenge #5

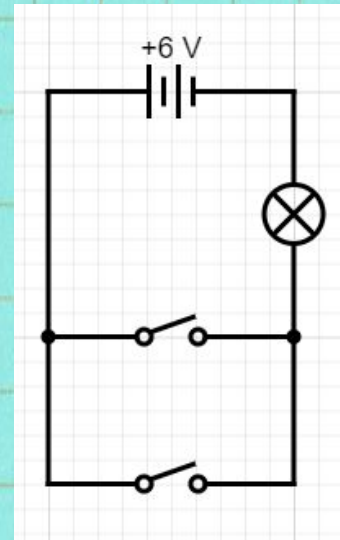

Suggested circuit

Battery, 2 switches and a bulb



How circuit works

The switches are wired in parallel. Either switch completes a circuit allowing current to flow through the bulb

Circuit setup using components



Link to video of circuit in action

<https://youtu.be/aqNaZnm48JQ>

