
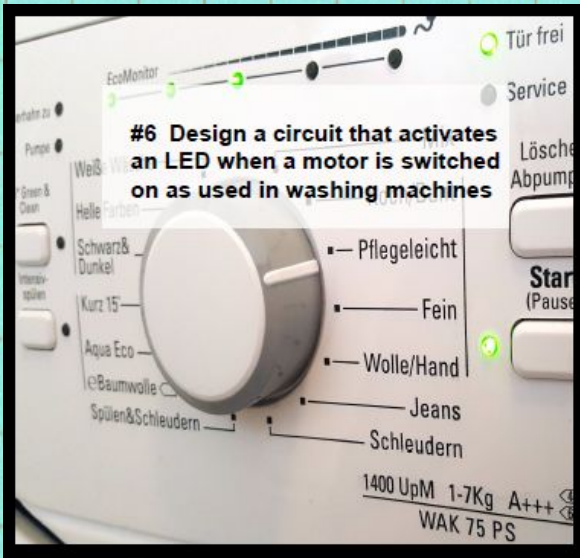


Challenge #6

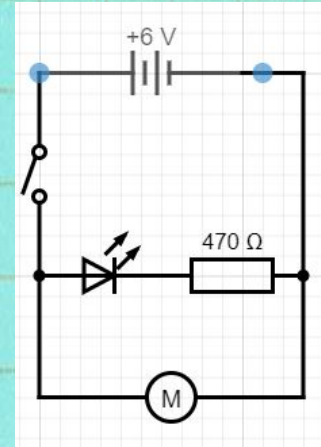

Suggested circuit
Battery, resistor, LED,
Motor and switch



How circuit works

The motor and LED are connected in parallel. The LED has a resistor in series to protect it. When the switch is closed current flows through both the LED and motor.

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/RAqXavTH70w>

