
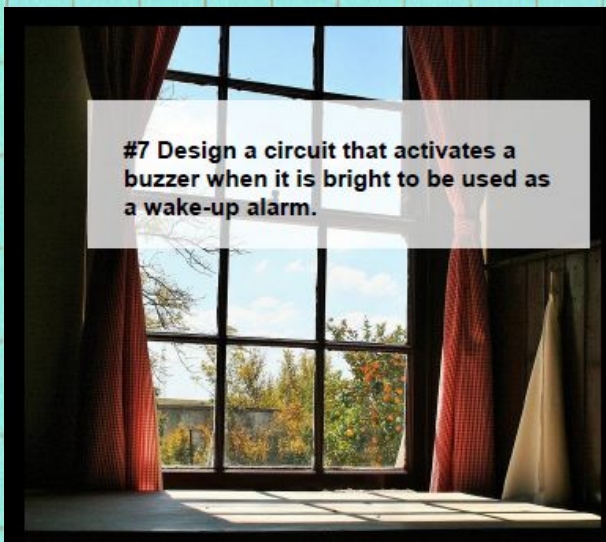


Challenge #7

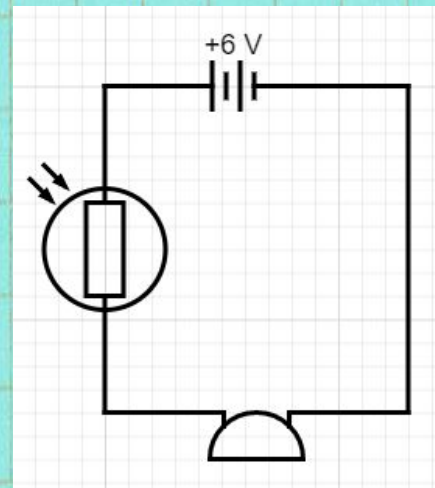

Suggested circuit

Battery, LDR and buzzer



How circuit works

When light falls on the LDR its resistance decreases allowing current to flow through the buzzer

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/IUT-3eODTGE>

