
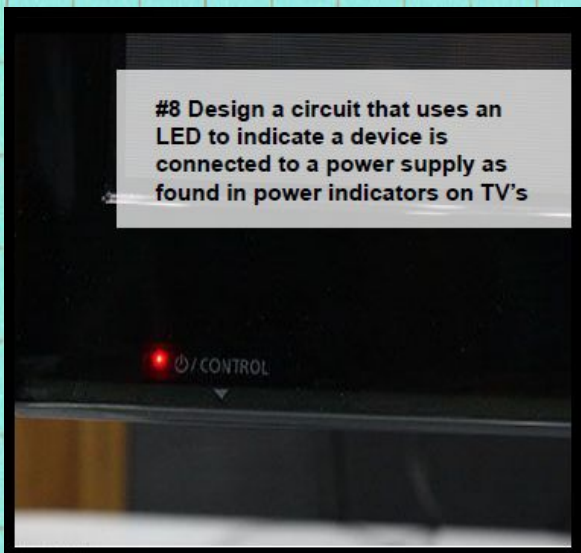


Challenge #8

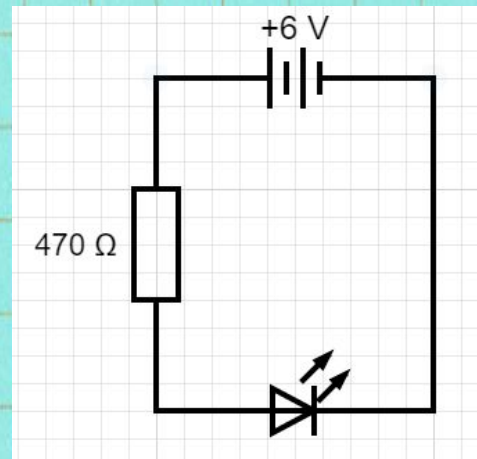


Suggested circuit
Battery, resistor, LED



How circuit works

The resistor produces light when a current passes through it. Resistors use very little power and must have a resistor in series to protect them.

Circuit setup using components

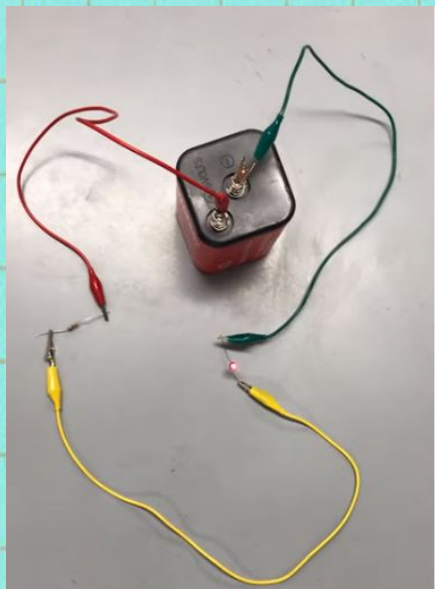

Link to video of circuit in action

<https://youtu.be/A5O05gNThhl>

