
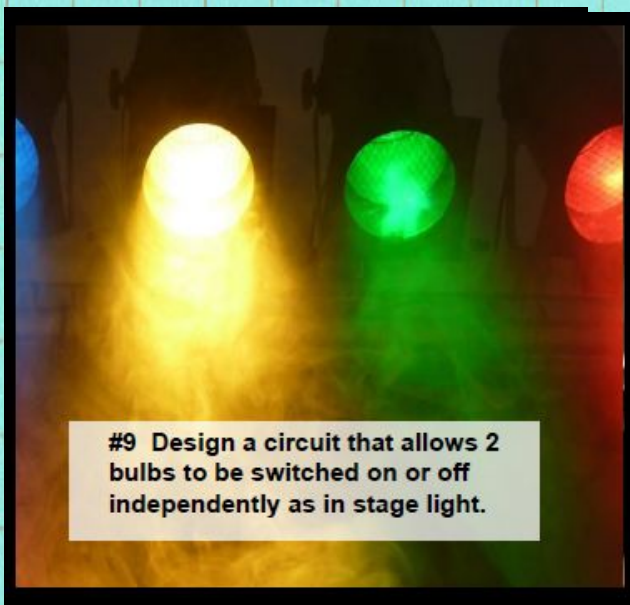


Challenge #9

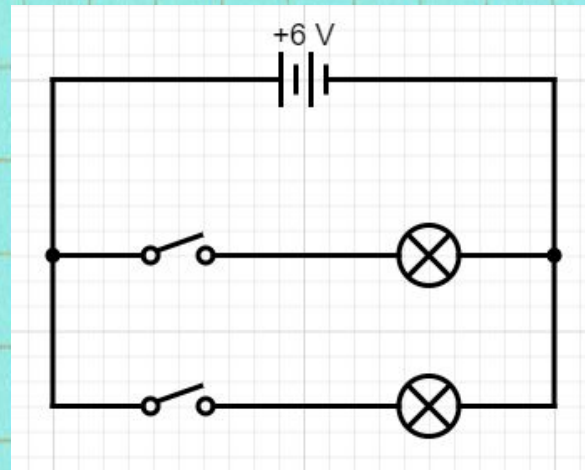


Suggested circuit
Battery, 2 switches
and 2 bulbs



How circuit works

Each bulb has a switch in series. Both bulb+switch systems are connected in parallel.

Circuit setup using components

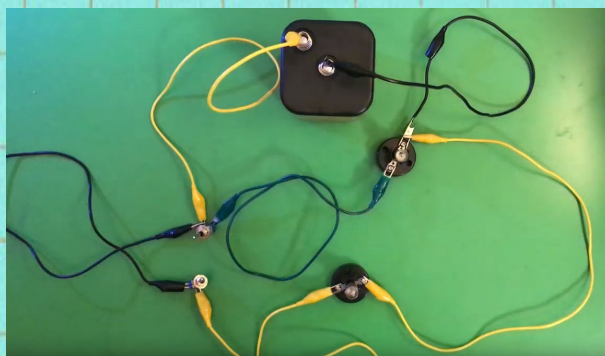

Link to video of circuit in action

https://youtu.be/H28a2_1B2RM

