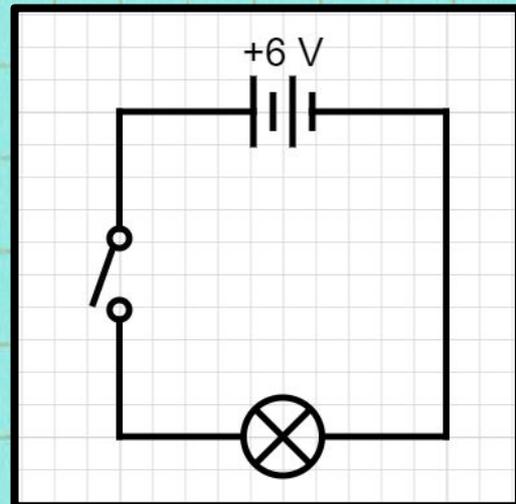


## Challenge #1



### Suggested circuit


Battery, switch and bulb



### How circuit works

Closing the switch allows current to flow around the circuit lighting the bulb.

### Circuit setup using components

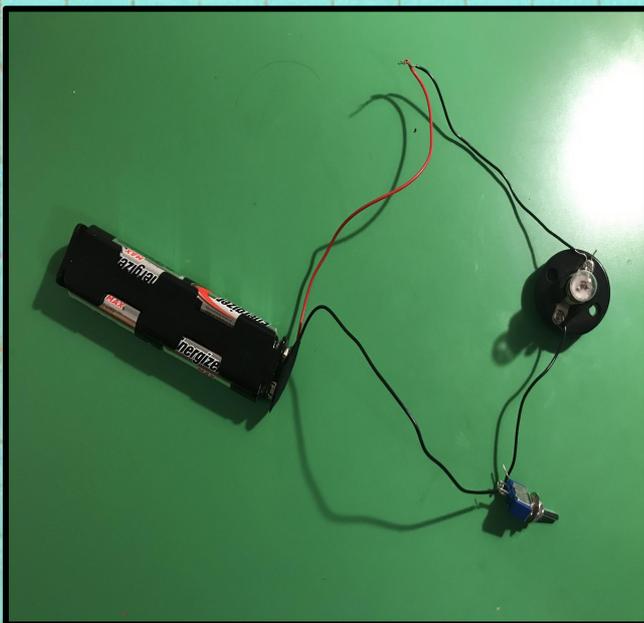


### Link to video of circuit in action

<https://youtu.be/f139wZft1xg>




## Challenge #2

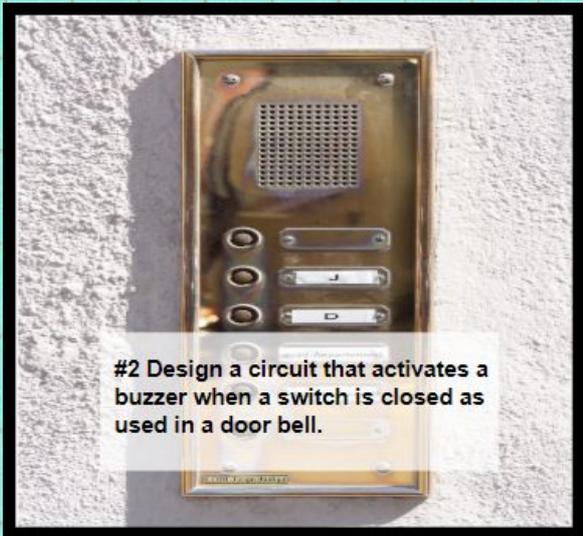

### Suggested circuit


Battery, switch and buzzer

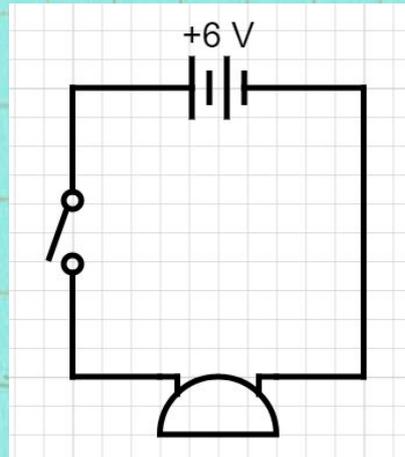

### How circuit works

Closing the switch allows current to flow around the circuit causing the buzzer to make a sound

### Circuit setup using components

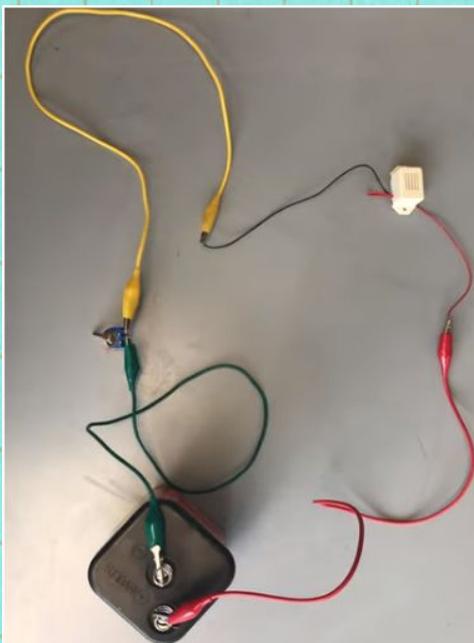


### Link to video of circuit in action

[https://youtu.be/iHa\\_Gj70CHI](https://youtu.be/iHa_Gj70CHI)




## Challenge #3

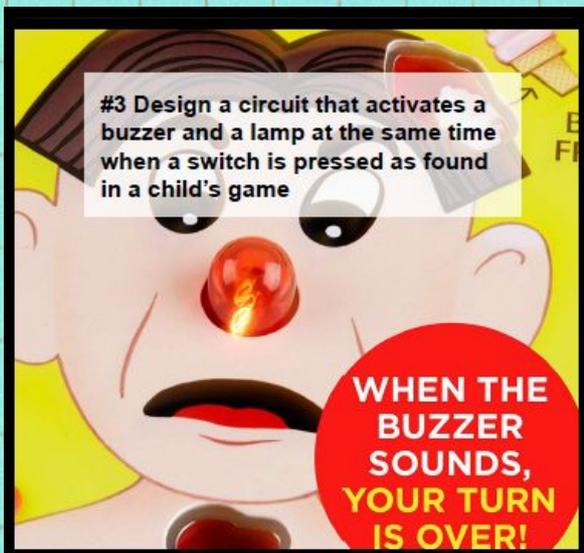

### Suggested circuit


Battery, switch, buzzer and bulb

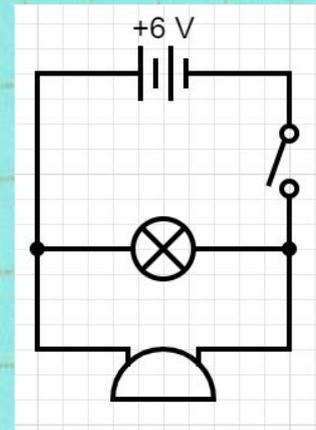

### How circuit works

The bulb and buzzer are wired in parallel. Closing the switch allows current to flow around the circuit causing the buzzer to make a sound and the bulb to light.

### Circuit setup using components

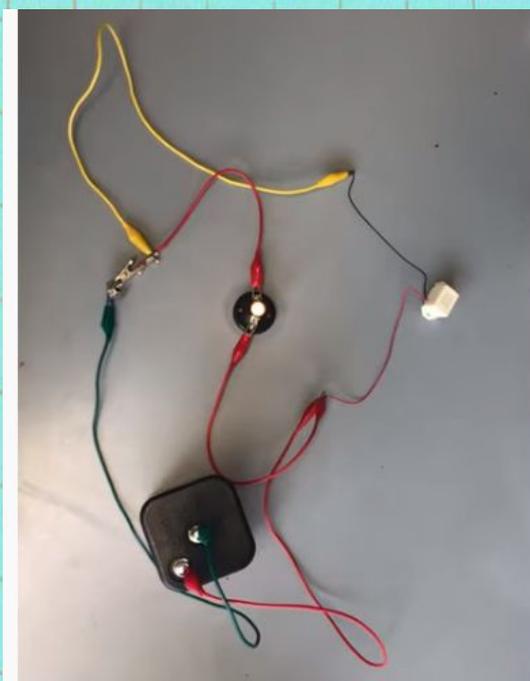

### Link to video of circuit in action

<https://youtu.be/WyHF6dObxao>




## Challenge #4



### Suggested circuit

Battery, motor and thermistor

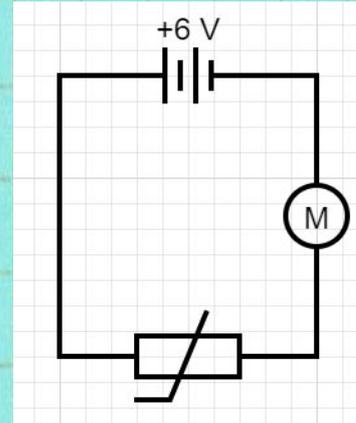

### How circuit works

As the temperature increases the resistance of the thermistor decreases. At high temperature the resistance is low enough to allow a large current to flow and activate the motor.

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/yIIIT8K5h7CE>




## Challenge #5

#5 Design a circuit that turns on a bulb when either of 2 switches is pressed as found in car interior lights.



### Suggested circuit

Battery, 2 switches and a bulb

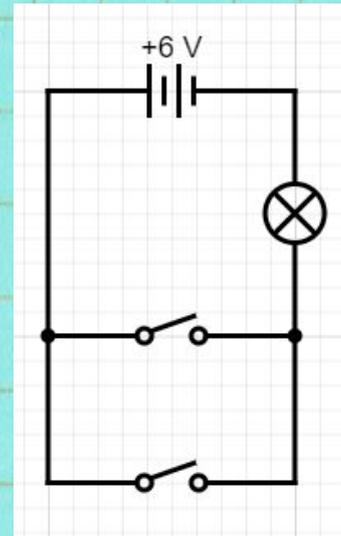

### How circuit works

The switches are wired in parallel. Either switch completes a circuit allowing current to flow through the bulb

### Circuit setup using components




### Link to video of circuit in action


<https://youtu.be/aqNaZnm48JQ>



## Challenge #6

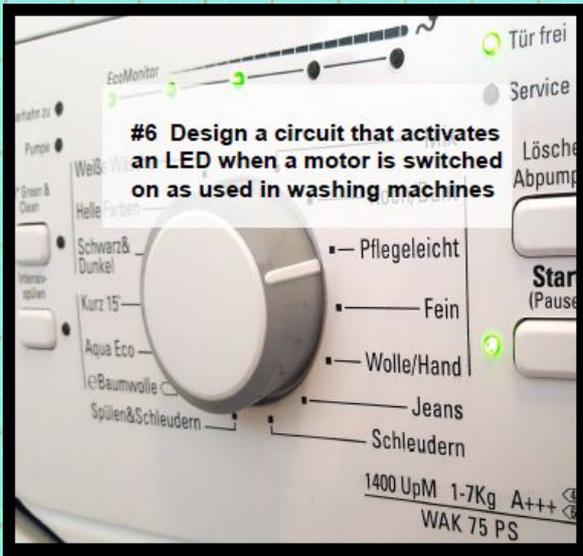

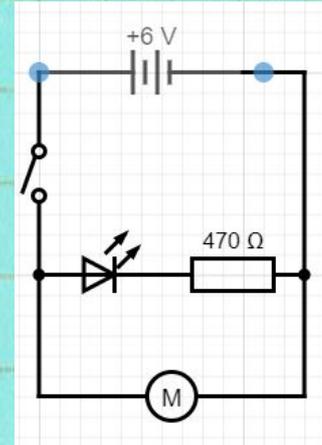**Suggested circuit**  
Battery, resistor, LED,  
Motor and switch




### How circuit works

The motor and LED are connected in parallel. The LED has a resistor in series to protect it. When the switch is closed current flows through both the LED and motor.


**Circuit setup using components**

**Link to video of circuit in action**

<https://youtu.be/RAqXavTH70w>

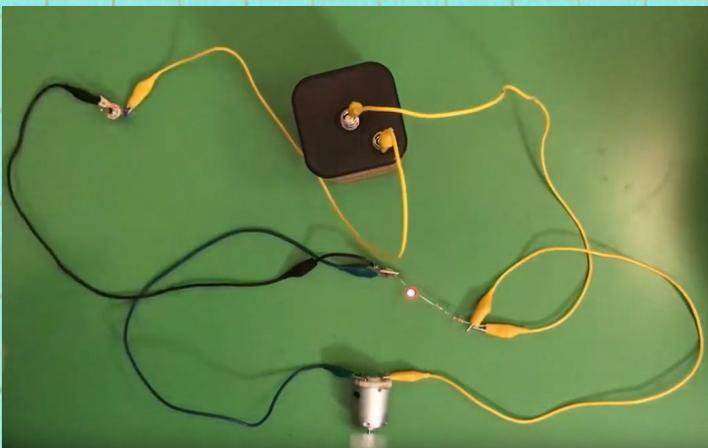


## Challenge #7

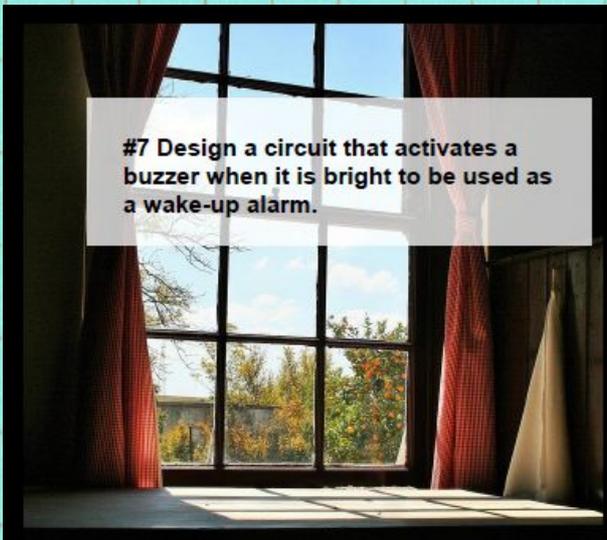

### Suggested circuit

Battery, LDR and buzzer

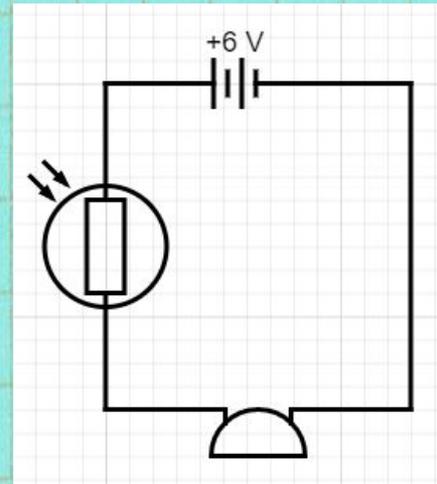


### How circuit works

When light falls on the LDR its resistance decreases allowing current to flow through the buzzer


Circuit setup using components

Link to video of circuit in action


<https://youtu.be/IUT-3eODTGE>

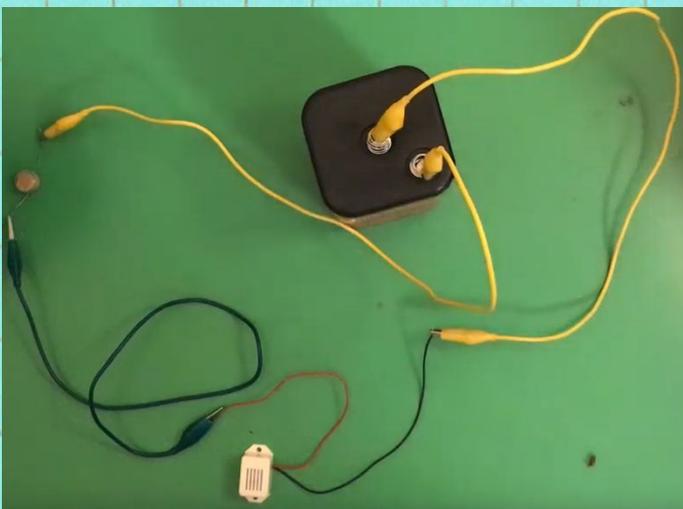

## Challenge #8

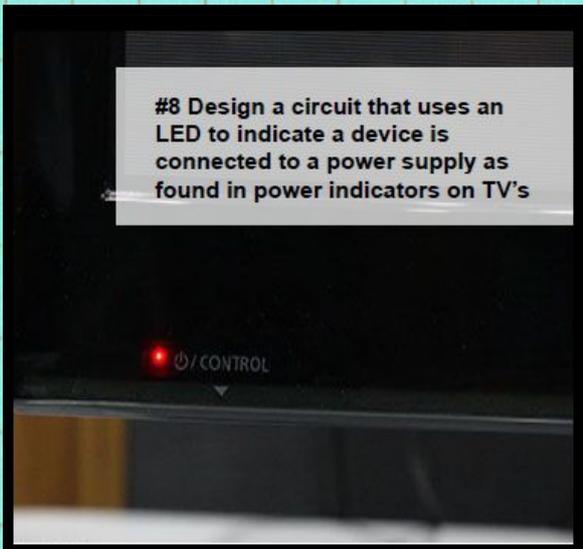

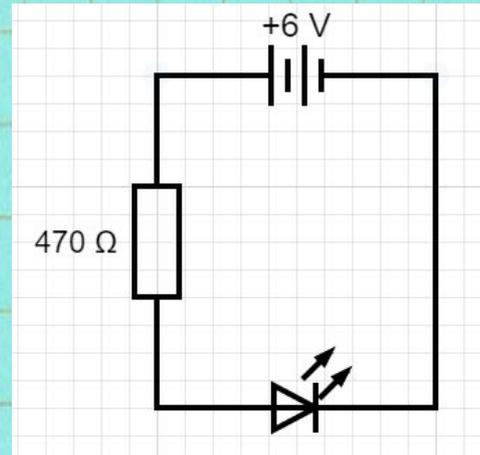
**Suggested circuit**  
Battery, resistor, LED



### How circuit works

The resistor produces light when a current passes through it. Resistors use very little power and must have a resistor in series to protect them.

**Circuit setup using components**

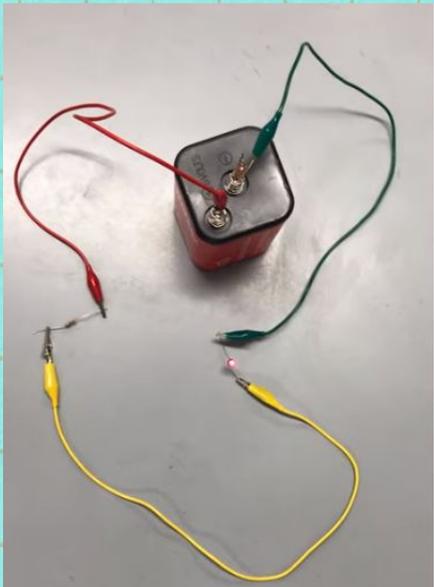


**Link to video of circuit in action**


<https://youtu.be/A5O05gNThhl>



## Challenge #9

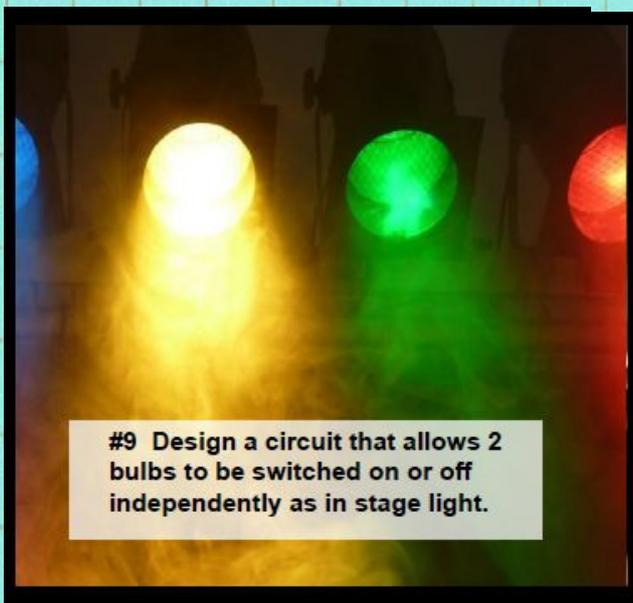

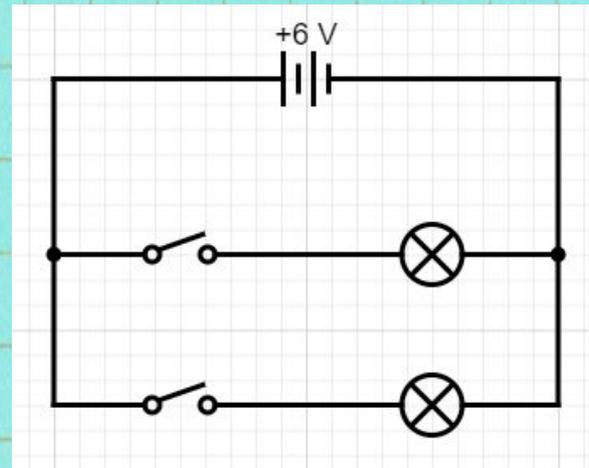
**Suggested circuit**  
Battery, 2 switches  
and 2 bulbs



### How circuit works

Each bulb has a switch in series. Both bulb+switch systems are connected in parallel.

**Circuit setup using components**

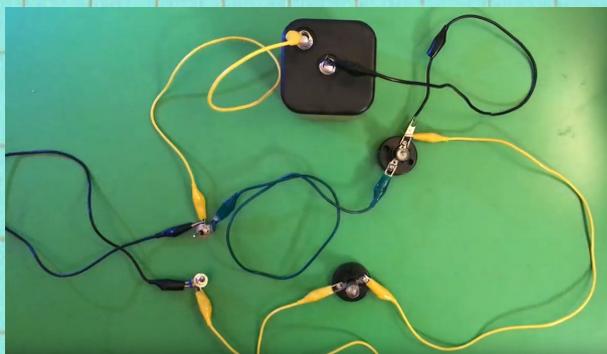

**Link to video of circuit in action**


[https://youtu.be/H28a2\\_1B2RM](https://youtu.be/H28a2_1B2RM)



## Challenge #10


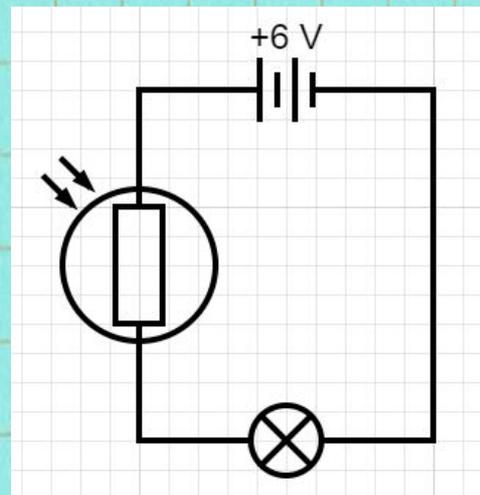
### Suggested circuit Battery, LDR and bulb




### How circuit works

In bright light the LDR has low resistance and allows current to flow through the bulb. In darkness the LDR has a high resistance and the flow of current through the bulb is reduced.

### Circuit setup using components

### Link to video of circuit in action


<https://youtu.be/l3NZnNVLDIU>

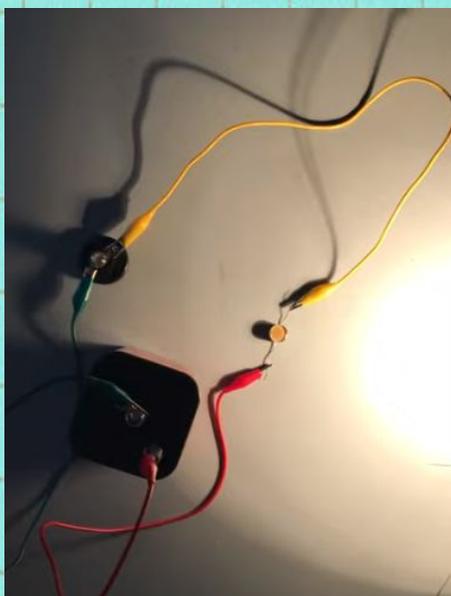
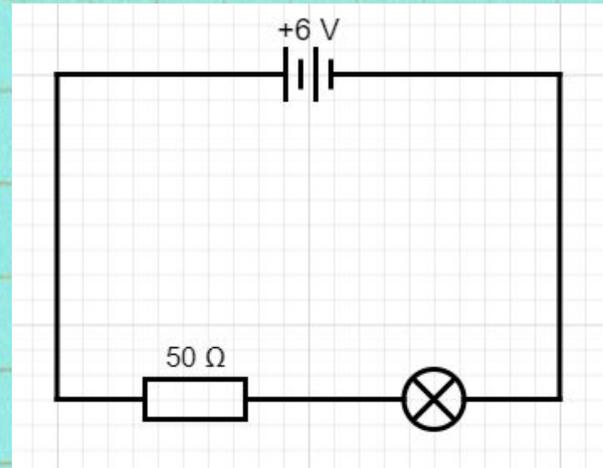
## Challenge #11



**Suggested circuit**  
Battery, resistor and bulb



### How circuit works

The resistor reduces the flow of current through the bulb

**Circuit setup using components**




**Link to video of circuit in action**


<https://youtu.be/da7hbxg91gw>



## Challenge #12

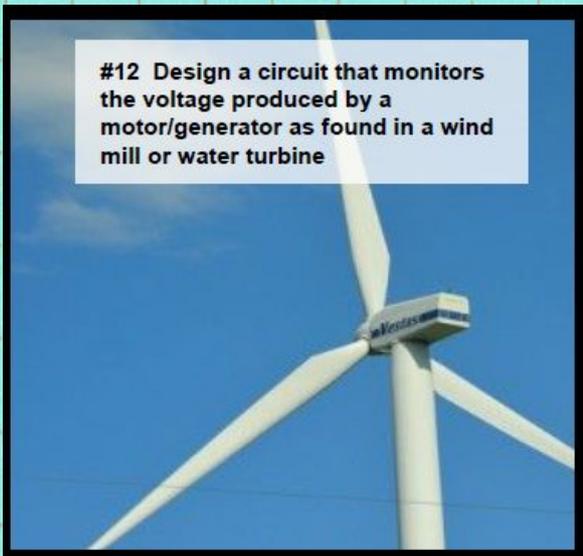
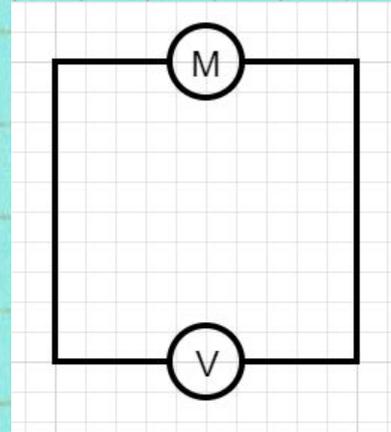
### Suggested circuit Motor and voltmeter



### How circuit works

Motors can act as generators. When the motor is turned a voltage or potential difference is produced which can be measured with a voltmeter. The faster the motor is turned the higher the voltage produced.

### Circuit setup using components



### Link to video of circuit in action

<https://youtu.be/hUNXavame88>




## Challenge #13



### Suggested circuit


Battery, variable resistor and motor

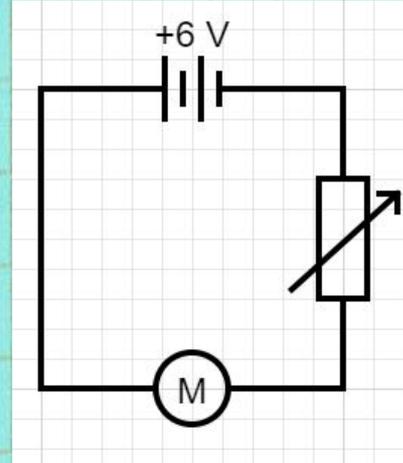

### How circuit works

As the resistance of the variable resistor is decreased, the current through the motor increases and it turns faster.

### Circuit setup using components

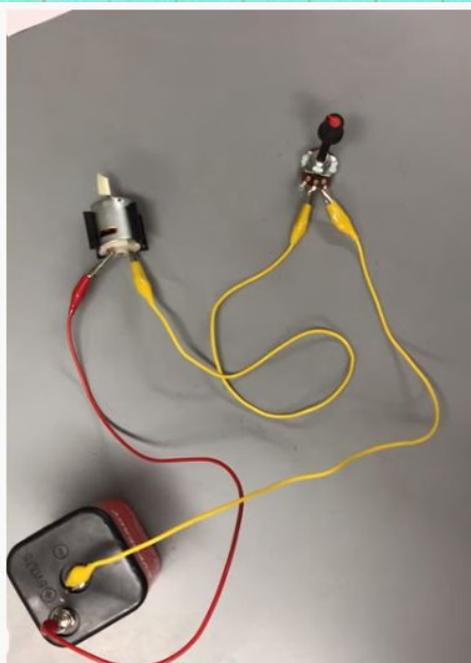


### Link to video of circuit in action

<https://youtu.be/cgZfzWLBzr8>




## Challenge #14

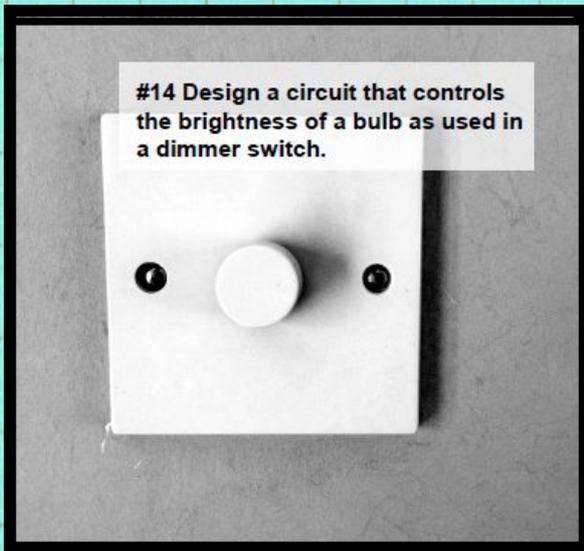

### Suggested circuit


Battery, variable resistor and bulb

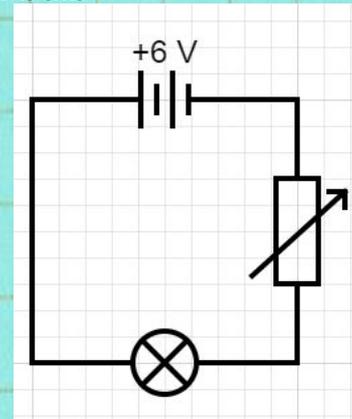

### How circuit works

As the resistance of the variable resistor is decreased, the current through the lamp increases and it becomes brighter.

### Circuit setup using components

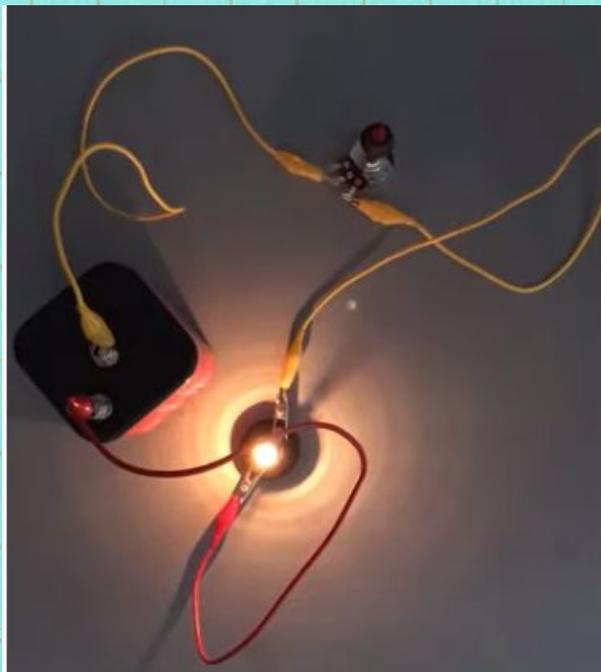


### Link to video of circuit in action

<https://youtu.be/Fvpzsn0ypqE>




## Challenge #15

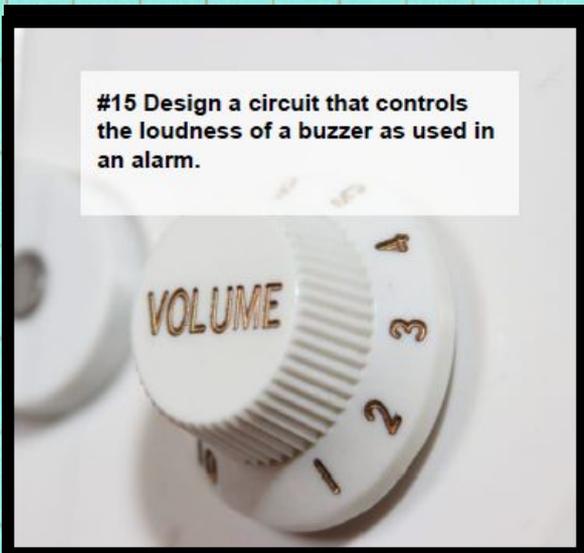

### Suggested circuit


Battery, variable resistor and buzzer.

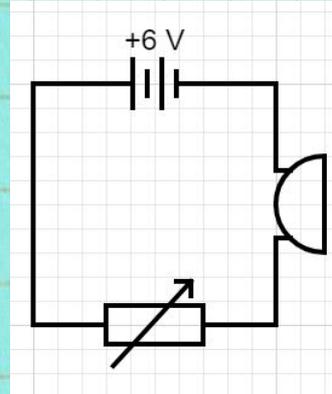

### How circuit works.

As the resistance of the variable resistor is decreased, the current through the buzzer increases and it becomes louder.

### Circuit setup using components

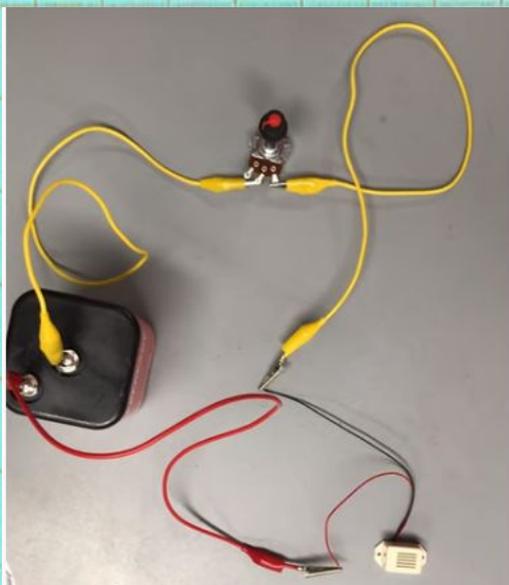

### Link to video of circuit in action

[https://youtu.be/S\\_qDZ7LUxRc](https://youtu.be/S_qDZ7LUxRc)




## Challenge #16



### Suggested circuit


Battery, diode and motor

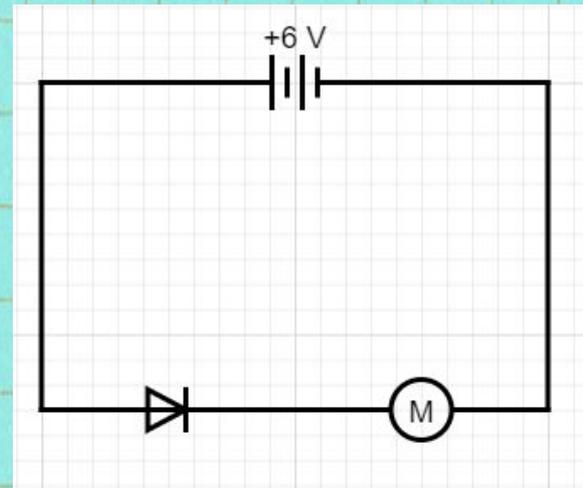

### How circuit works

Diodes only allow current to flow in one direction.

### Circuit setup using components

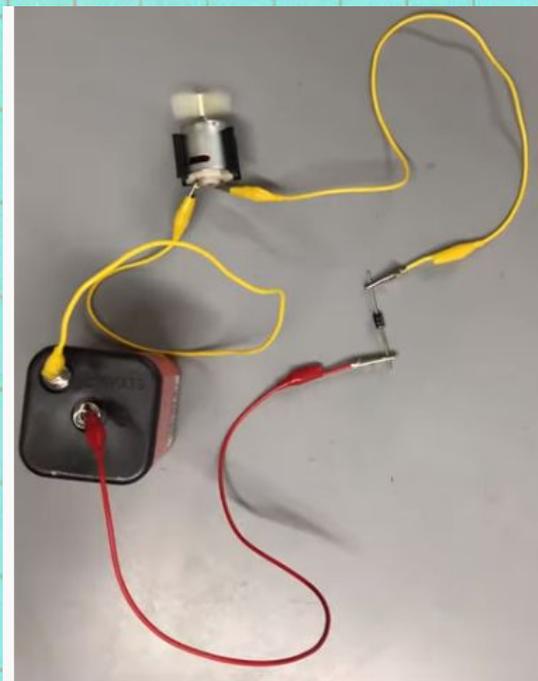

### Link to video of circuit in action

<https://youtu.be/9Fwd9vNCLPY>




## Challenge #17



### Suggested circuit


Battery, bulb, motor and voltmeter.

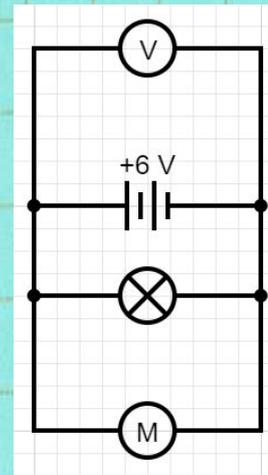

### How circuit works

The voltmeter is connected in parallel to the battery. The motor and lamp are connected in parallel to the battery also.

### Circuit setup using components

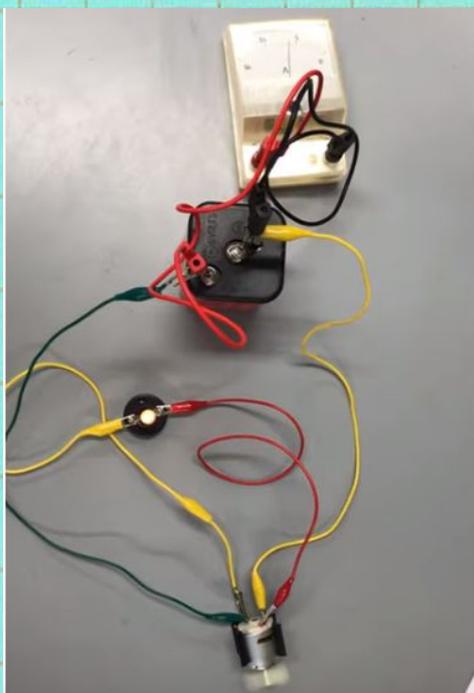


### Link to video of circuit in action


<https://youtu.be/Rv8Wlwl2o3w>



## Challenge #18

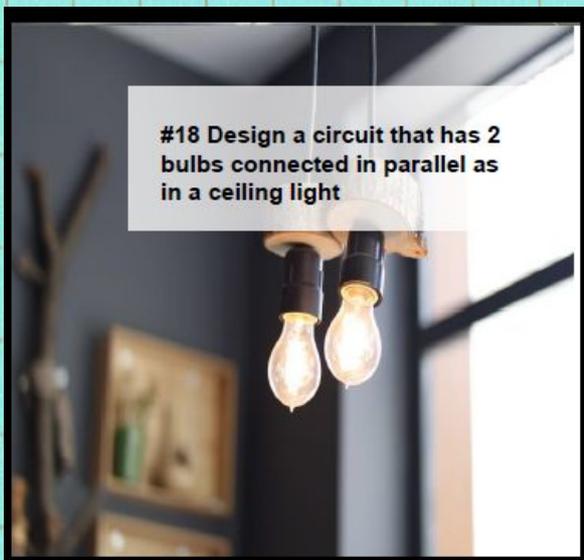

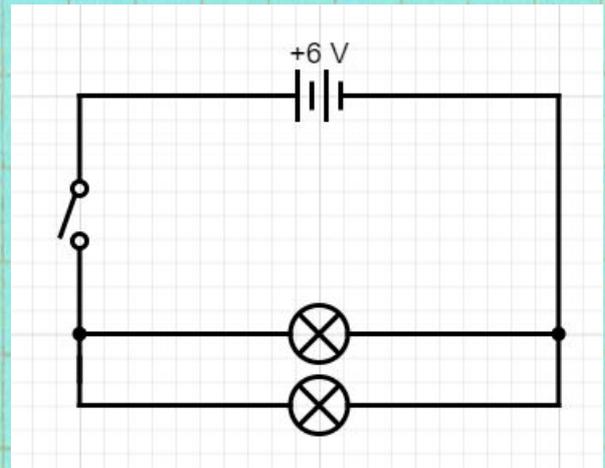**Suggested circuit**  
Battery, switch and 2 bulbs




### How circuit works

Closing the switch allows current to flow through both bulbs connected in parallel. Bulbs in parallel are brighter than bulbs in series .


**Circuit setup using components**

**Link to video of circuit in action**


<https://youtu.be/KJIVL5CrcEg>

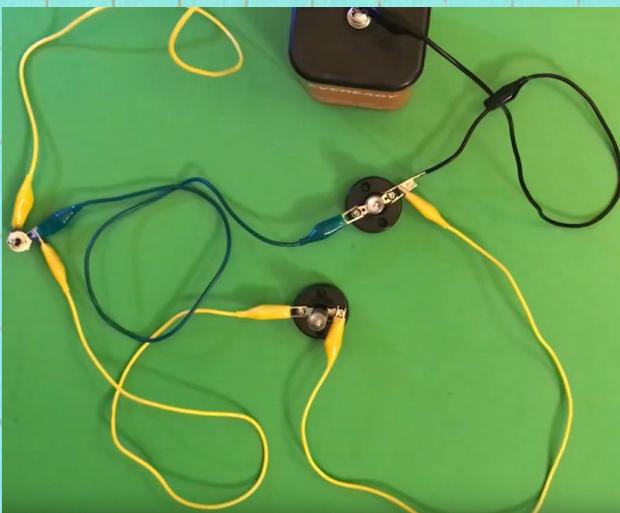

## Challenge #19

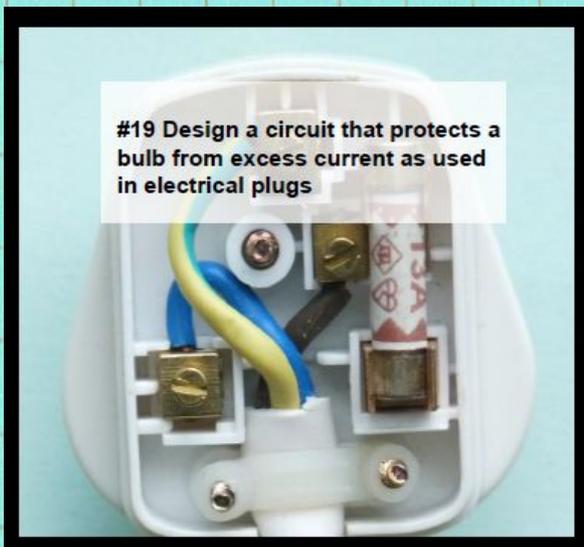

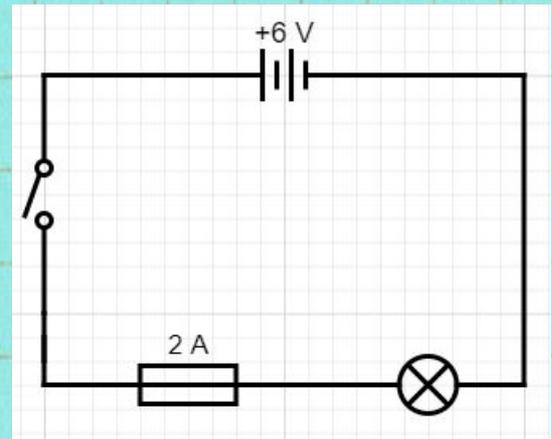
**Suggested circuit**  
Battery, switch, fuse and bulb



### How circuit works

The fuse is connected in series with the bulb. The small wire inside the fuse will melt and break the circuit if the current is too great.

**Circuit setup using components**

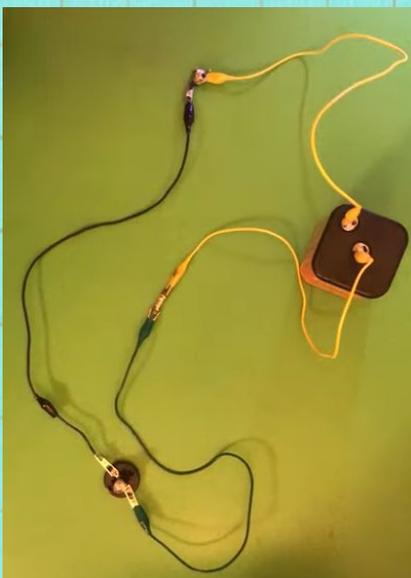


**Link to video of circuit in action**

<https://youtu.be/gwc04FifcGw>




## Challenge #20

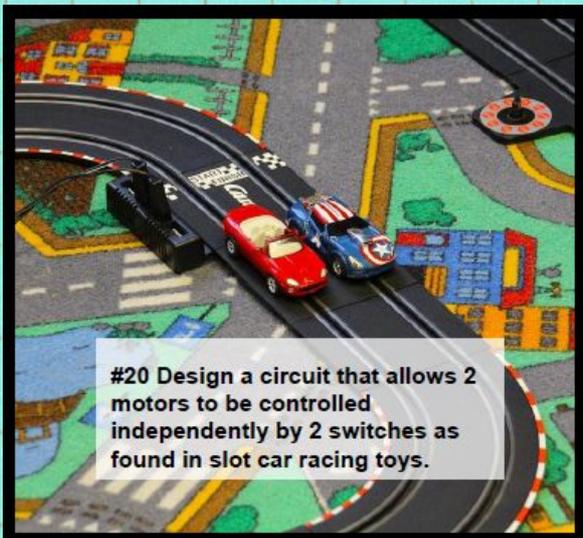

### Suggested circuit


Battery, 2 switches and 2 motors

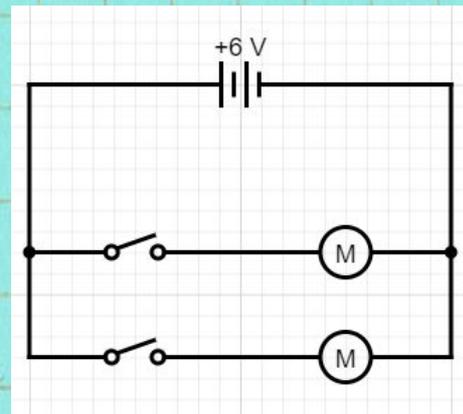

### How circuit works

Each motor has a switch in series. Both motor+switch systems are connected in parallel.

Circuit setup using components

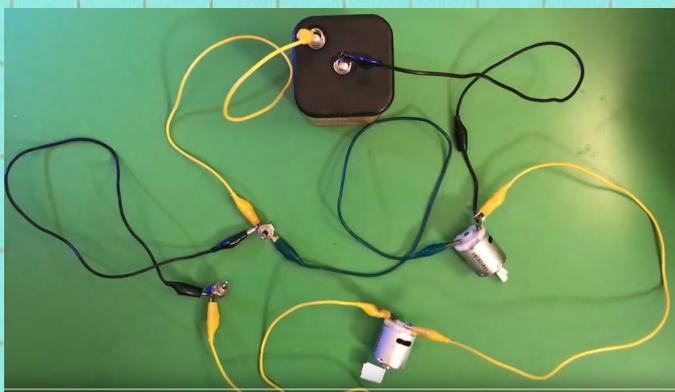

Link to video of circuit in action

<https://youtu.be/lvizmDUy-i4>




## Challenge #21



### Suggested circuit

Battery, 2 switches and motor

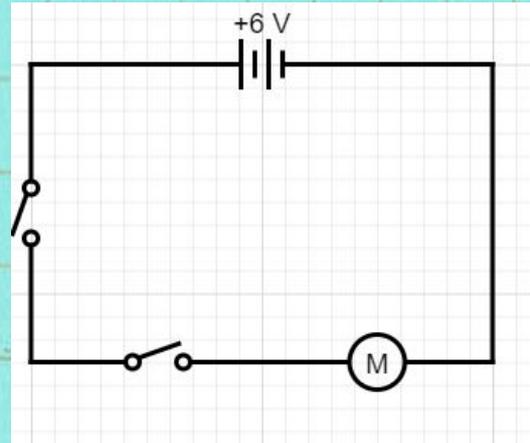


### How circuit works

Both switches are connected in series with a motor. Both switches must be closed for current to pass through the motor


Circuit setup using components

Link to video of circuit in action


<https://youtu.be/suEDYMvGma8>

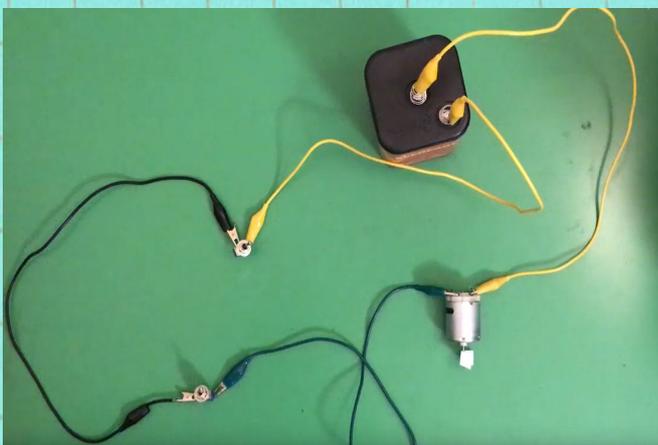

## Challenge #22

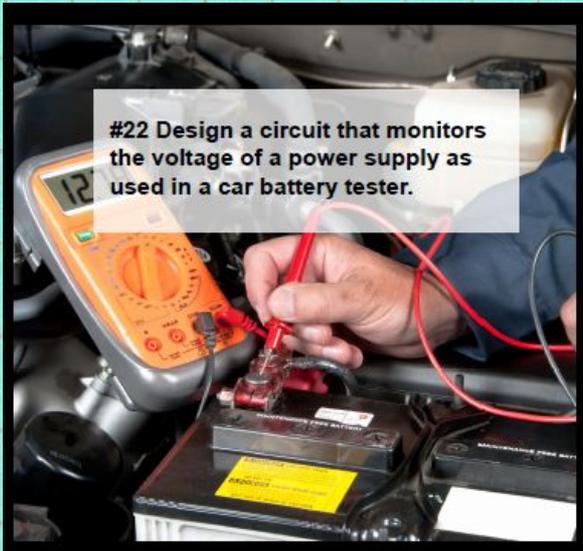

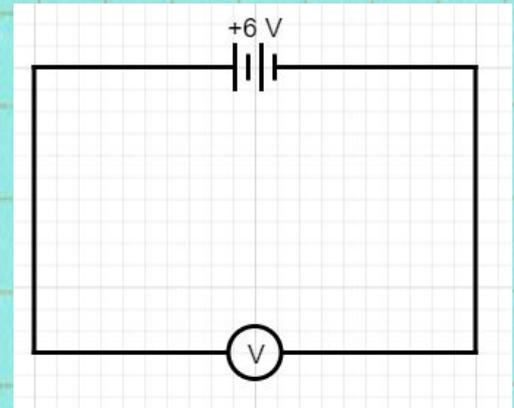**Suggested circuit**  
Battery, voltmeter



### How circuit works

Voltmeters are always connected in parallel to devices.

**Circuit setup using components**

**Link to video of circuit in action**

<https://youtu.be/yEMRJCmMisl>




## Challenge #23



### Suggested circuit


Battery, switch, ammeter and 2 bulbs.

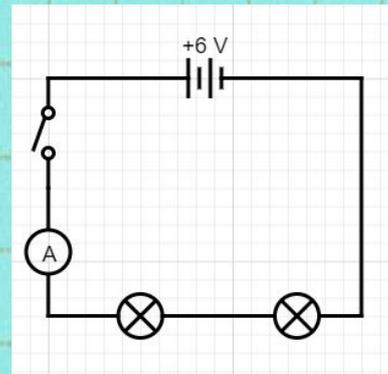

### How circuit works

Both bulbs are connected in series to an ammeter which monitors the current flowing in a circuit. Ammeters are always connected in series in a circuit.

### Circuit setup using components

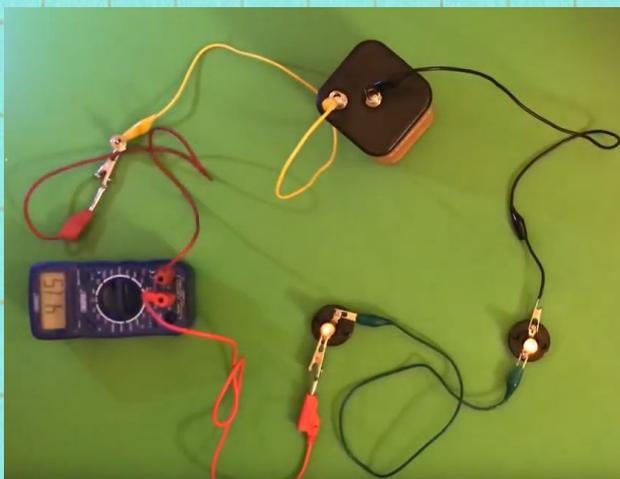


### Link to video of circuit in action

[https://youtu.be/rPZwl\\_IA8k0](https://youtu.be/rPZwl_IA8k0)




## Challenge #24

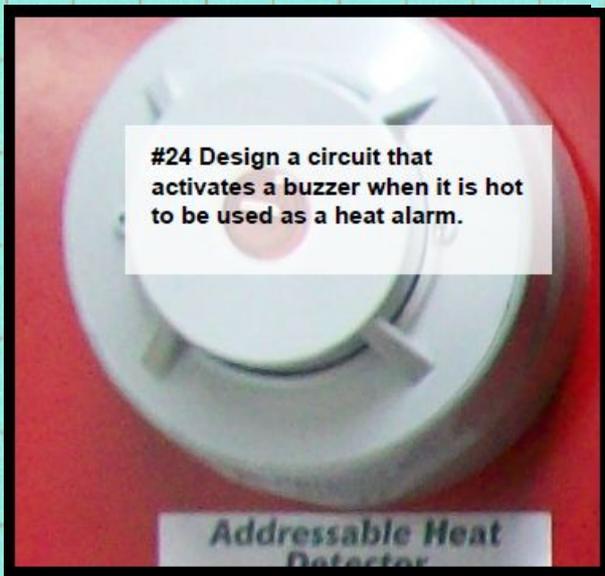

### Suggested circuit

Battery, thermistor and buzzer

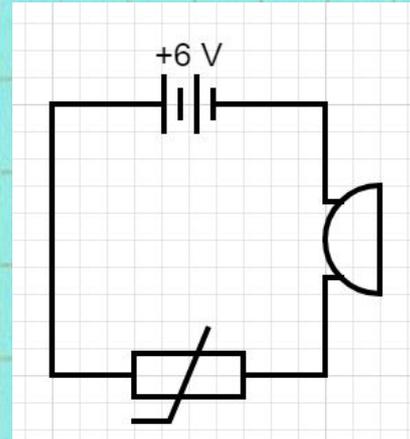

### How circuit works

As the temperature increases the resistance of the thermistor decreases. At high temperature the resistance is low enough to allow a large current to flow and activate the buzzer

Circuit setup using components

Link to video of circuit in action

<https://youtu.be/OK542vygi5k>

